


Assignment 2

1. what is Sum of the product?
 Ans. It consists of two or more AND terms that are ORed together. Each of these AND terms AND terms can contain any number of variable in either true or its complement form
 $(A.B) + (\bar{A}.B)$

$\Sigma m(0, 2, 3, 4, 5, 6)$

A \ BC	00	01	11	10
0	1 ₀	0 ₁	1 ₃	1 ₂
1	1 ₄	1 ₅	0 ₇	1 ₆

$$f = \bar{C} + A\bar{B} + \bar{A}B$$

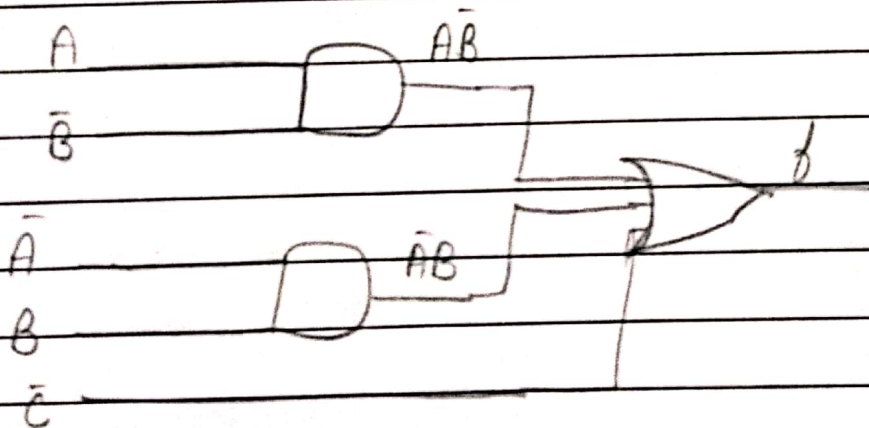


$$f = \bar{A}\bar{B}C + AB\bar{C}$$

what is product of the sum
~~for~~ It consists of two or more OR terms that are ANDed together. Each of these OR terms can contain any number of variable in either true or its complemented form.

$$(A+B) (\bar{A}+B)$$

A \ BC	00	01	10	11
0	1	0	1	0
1	0	1	0	1

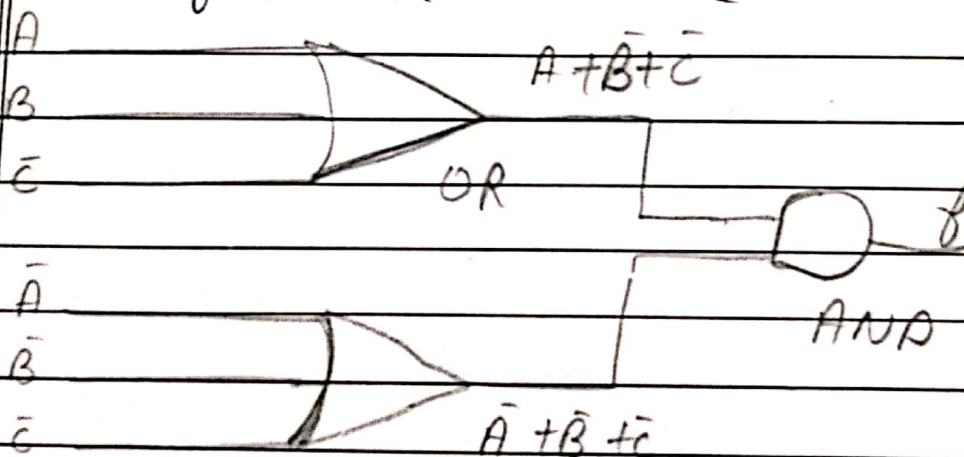
$$f = (A+B+\bar{C}) \cdot (\bar{A}+\bar{B}+\bar{C})$$



What is encoder?

Encoder is a logic circuit which performs the opposite action of the Decoder. An encoder has a number of input lines, only one of which is activated at a time. At the output is displayed a value corresponding to the activated input. An encoder has 2^n input lines and n output lines.

$$8 = 2^3 = 2^3$$

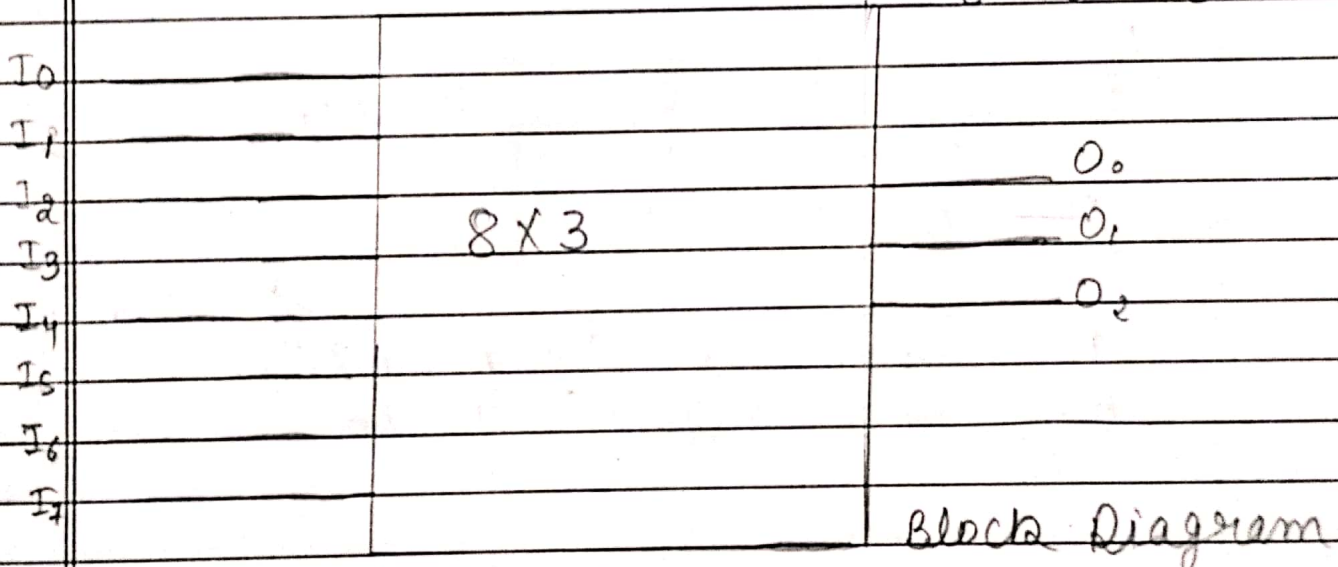

Types of Encoder:


Priority Encoder

Decimal to BCD Encoder

Octal to Binary Encoder

Hex to Binary Encoder.

Design 4x2 encoder

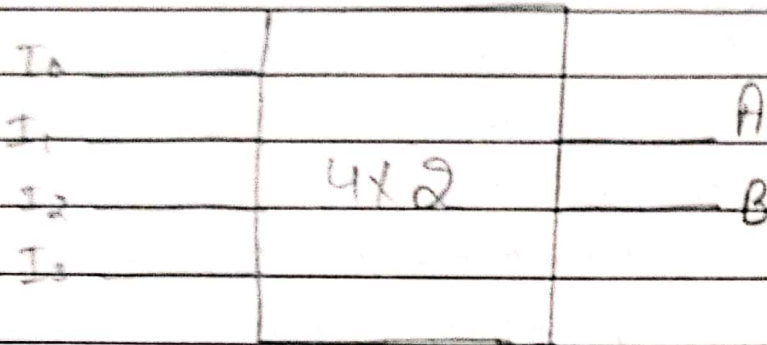


Block diagram


Input				Output	
I_0	I_1	I_2	I_3	A	B
1	0	0	0	0	0
0	1	0	0	0	1
0	0	1	0	1	0
0	0	0	1	1	1

$$A = \bar{I}_0 \bar{I}_1 I_2 \bar{I}_3 + \bar{I}_0 \bar{I}_2 I_1 I_3$$
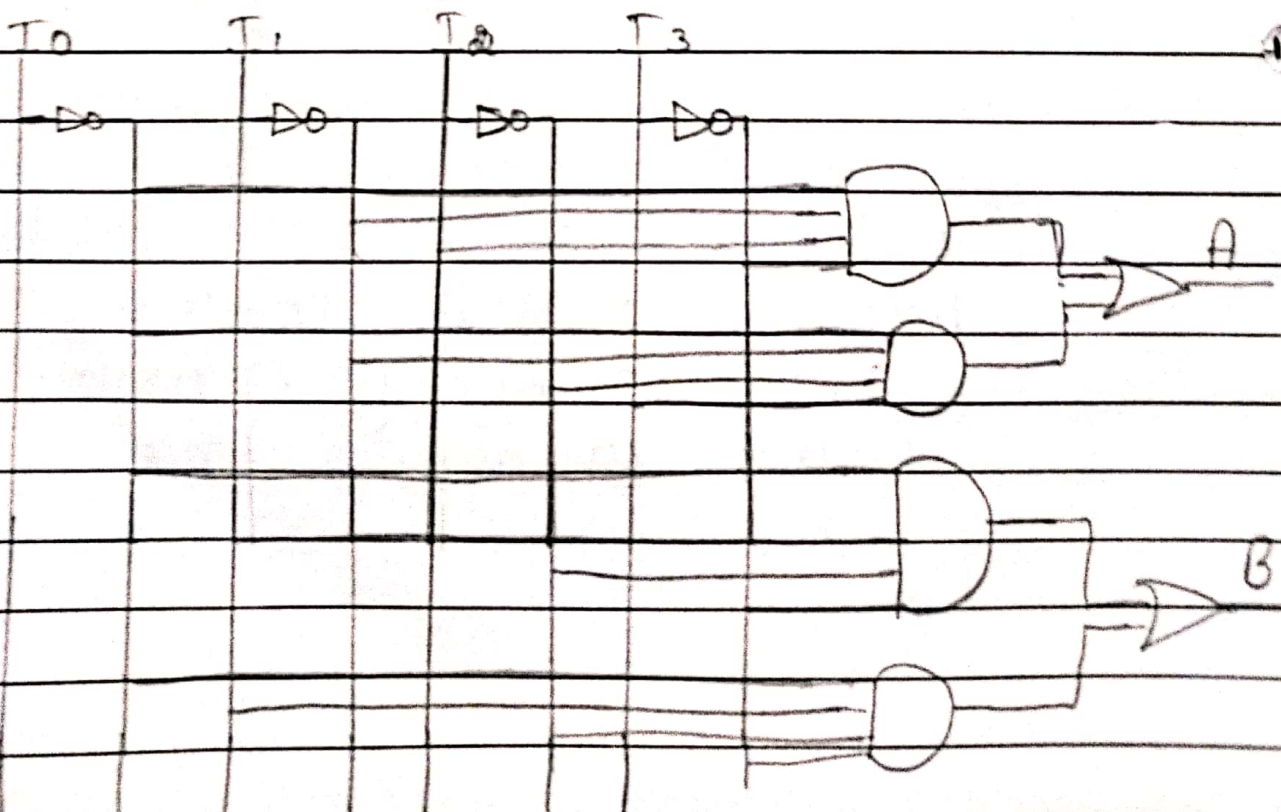
$$B = \bar{I}_0 I_1 \bar{I}_2 \bar{I}_3 + \bar{I}_0 \bar{I}_1 \bar{I}_2 I_3$$




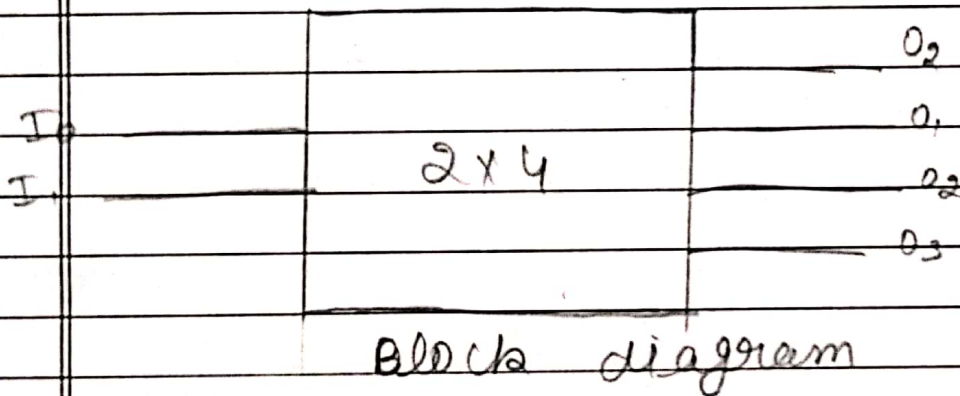Decoder: A decoder is a logic circuit that accepts a set of inputs that represent a binary number and activated that output which corresponding to the input binary number. A decoder has n inputs and an enable line and 2^n output lines.




Input			Output			
I_0	I_1	I_2	O_0	O_1	O_2	O_3
0	0		1	0	0	0
0	1		0	1	0	0
1	0		0	0	1	0
1	1		0	0	0	1

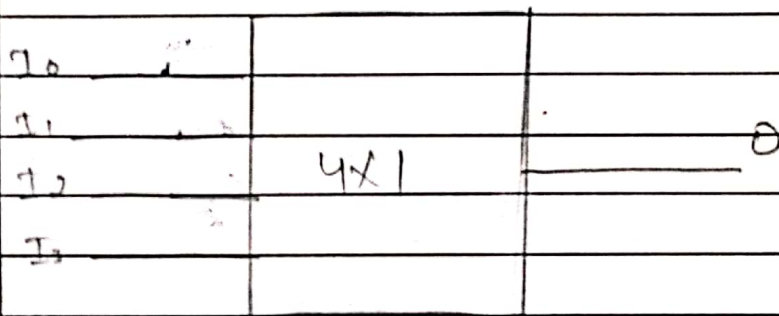multiplexer: A multiplexer is a logic circuit which accepts many inputs, but select only one input to be passed on to the output. It is sometimes referred to as a data selector, since it selects only one of the inputs. Multiplexer is also known as mux.




S_0	S_1	O
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

Logic Diagram

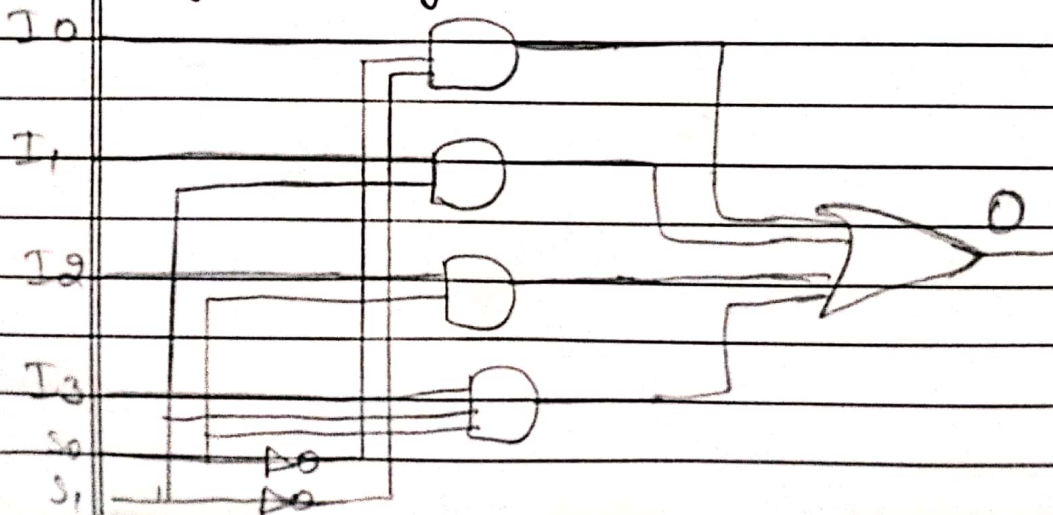


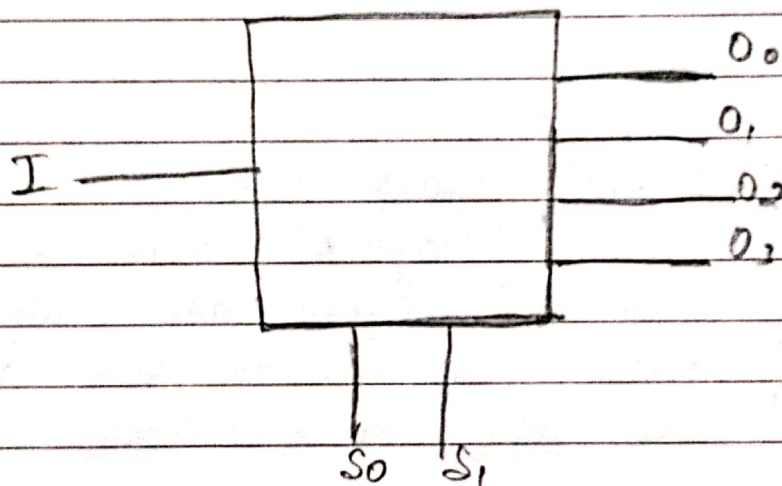De-multiplexer: A de-multiplexer performs the reverse operation of the multiplexer. It takes one single input and passes this to the output number specified by the select inputs. It is also called as Demux or Data Distributor.



S_0	S_1	Input	Outputs
0	0	1	O_0
0	1	1	O_1
1	0	1	O_2
1	1	1	O_3

Logic Diagram:

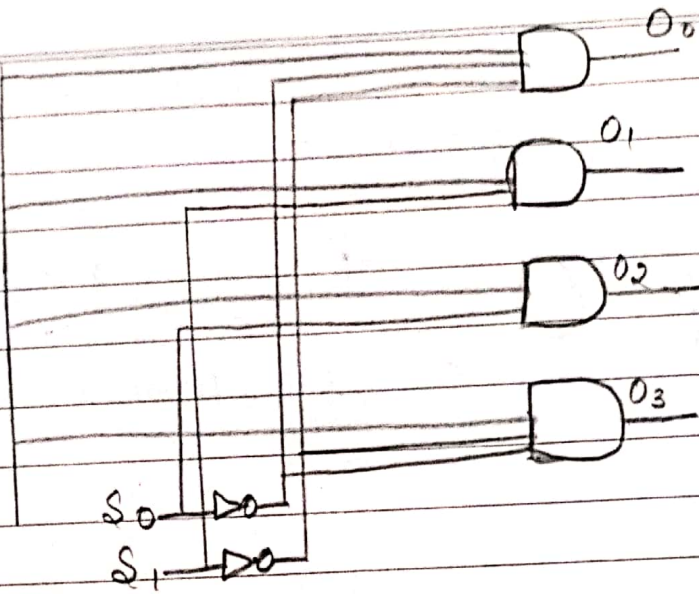

Half Adder: Half adder adds two binary digits and produces two binary outputs called sum and carry. In half adder the inputs are the augend (let's say 'A') and addend 'B'.



Input		Sum		Carry
A	B	S	C	
0	0	0	0	
0	1	1	0	
1	0	1	0	
1	1	0	1	

Sum


B	0	1
A		
0	0	1
1	1	0

$$S = \bar{A}B + A\bar{B}$$

Carry


B	0	1
A		
0	0	0
1	0	1

$$C = AB$$

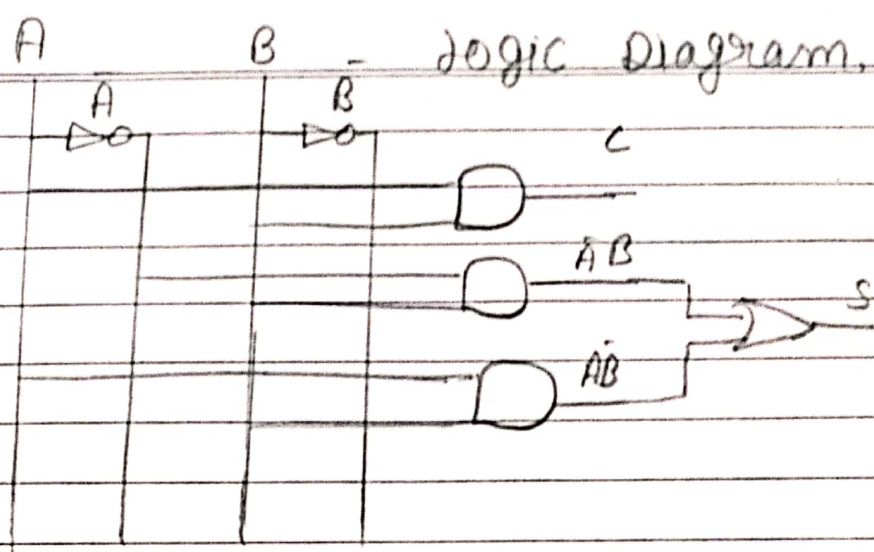

Full ~~adder~~ Adder:

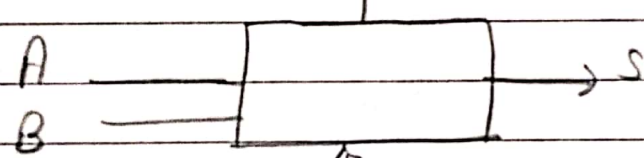Half - Adder is a simple circuit but not effective for adding more than two digits. when three bits need to be added, we used a full adder circuit (the third bit is the previous carry bit).



	BP	00	01	11	10
A	0	0	1	0	1
1	1	0	1	0	0

Sum

$$S = \bar{A}\bar{B}P + \bar{A}B\bar{P} + A\bar{B}\bar{P} + ABP$$

	BP	00	01	11	10
A	0	0	0	1	0
1	0	1	1	1	1

carry

$$\begin{aligned} &A\bar{B}P + ABP \\ &AP(B + \bar{B}) \\ &= AP \end{aligned}$$

A	B	P	S	C
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$\begin{aligned} & \bar{A}BP + ABP \\ &= BP(A + \bar{A}) \\ &= BP \end{aligned}$$

$$\begin{aligned} & ABP + AB\bar{P} \\ &= AB(P + \bar{P}) \\ &= AB \end{aligned}$$

$$C = AP + BP + AB$$

$$S = \bar{A}\bar{B}P + \bar{A}B\bar{P} + ABP + A\bar{B}\bar{P}$$

